

## Sirkuit <u>mekuivalen</u>

### Transmisi Daya Listrik

# Buku Rujukan Bab 5

#### SI EDITION



FIFTH EDITION

# POWER SYSTEM ANALYSIS & DESIGN

J. DUNCAN GLOVER
MULUKUTLA S. SARMA
THOMAS J. OVERBYE



### Persamaan Saluran Transmisi Terdistribusi

### **Parameter ABCD**

$$\begin{bmatrix} V_{\rm S} \\ I_{\rm S} \end{bmatrix} = \begin{bmatrix} A & B \\ \hline C & D \end{bmatrix} \begin{bmatrix} V_{\rm R} \\ I_{\rm R} \end{bmatrix}$$
 (5.2.33)

where

$$A = D = \cosh(\gamma l) \quad \text{per unit} \tag{5.2.34}$$


$$B = Z_c \sinh(\gamma l) \quad \Omega \tag{5.2.35}$$

$$C = \frac{1}{Z_c} \sinh(\gamma l) \quad S \tag{5.2.36}$$


$$\gamma = \sqrt{zy} \quad \mathrm{m}^{-1} \qquad \qquad Z_c = \sqrt{\frac{z}{y}} \quad \Omega$$


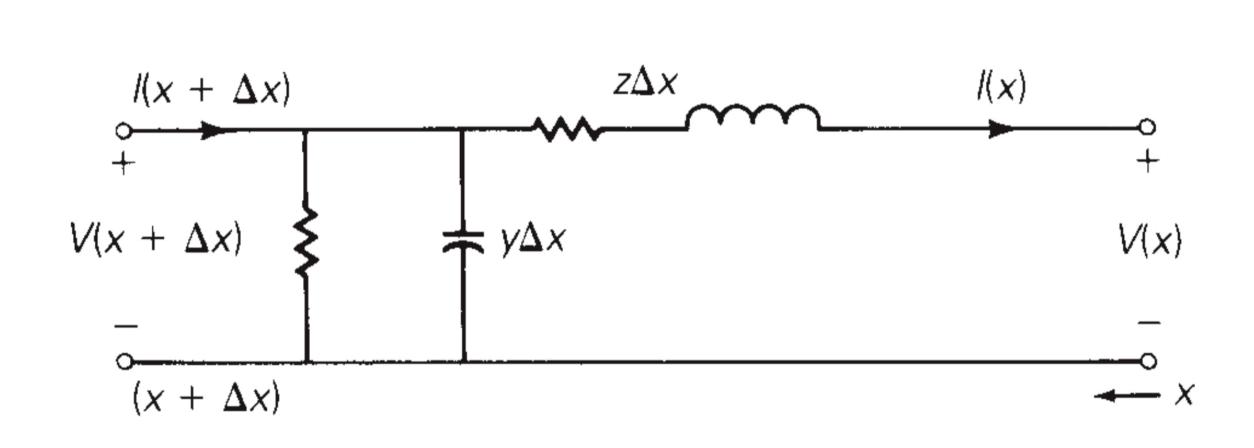
## Perbandingan Rangkaian Nominal dan $\pi$


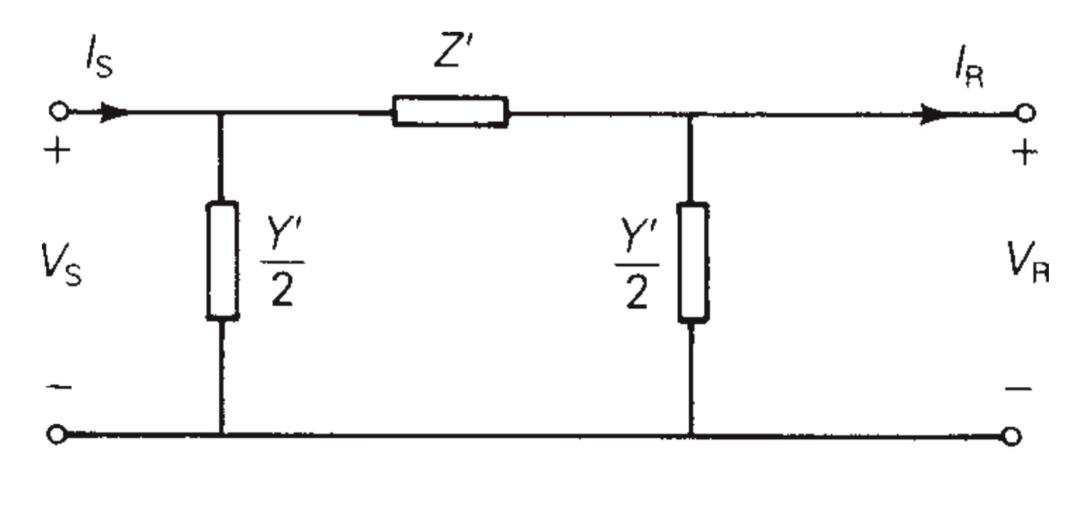
$$z = R + j\omega L$$
  $\Omega/m$   
 $y = G + j\omega C$   $S/m$ 




$$Z' = Z_c \sinh(\gamma \ell) = ZF_1 = Z \frac{\sinh(\gamma \ell)}{\gamma \ell}$$

$$\frac{Y'}{2} = \frac{\tanh(\gamma\ell/2)}{Z_c} = \frac{Y}{2}F_2 = \frac{Y}{2}\frac{\tanh(\gamma\ell/2)}{(\gamma\ell/2)}$$



### Rangkaian $\pi$ ekivalen

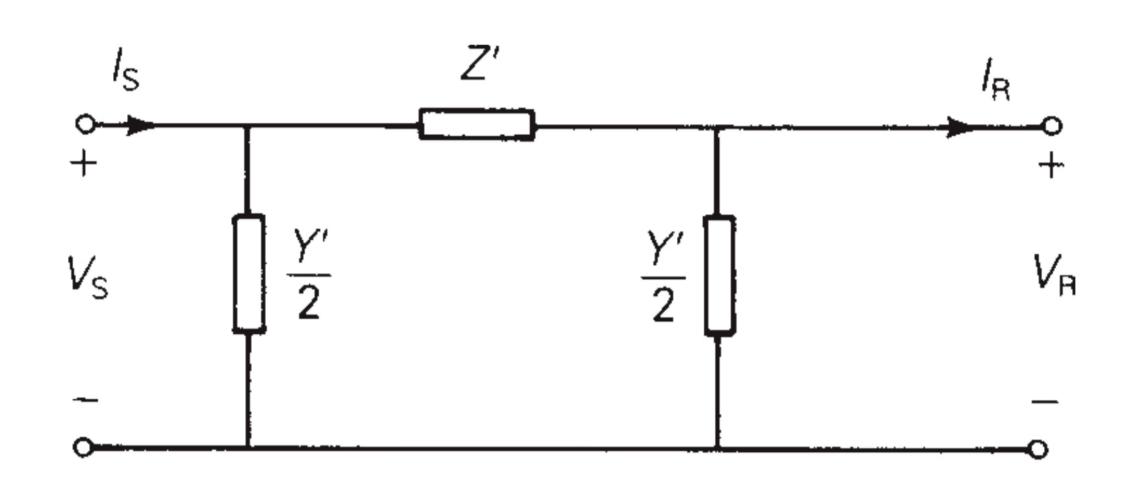

$$Z' = Z_c \sinh(\gamma \ell) = ZF_1 = Z \frac{\sinh(\gamma \ell)}{\gamma \ell}$$

$$\frac{Y'}{2} = \frac{\tanh(\gamma\ell/2)}{Z_c} = \frac{Y}{2}F_2 = \frac{Y}{2}\frac{\tanh(\gamma\ell/2)}{(\gamma\ell/2)}$$

